



上海交通大学  
Shanghai Jiao Tong University



# Project2 Approximate Adder Design

## Digital Integrated Circuit Design

TA1: Yuxuan Qin - [qinyuxuan@sjtu.edu.cn](mailto:qinyuxuan@sjtu.edu.cn);

TA2: Zihan Lian - [lianzihan@sjtu.edu.cn](mailto:lianzihan@sjtu.edu.cn);





# Outline



## 实验概述

- 加法器简介
- 近似计算加法器



## 实验要求



## 附录



# 半加器

两输入a、b，两输出s、cout

$$c_{out} = a \cdot b$$
$$s = a \oplus b$$

a	b	c <sub>out</sub>	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



两输入a、b，进位输入cin

$$\begin{aligned} c_{out} &= a \cdot b + a \cdot c_{in} + b \cdot c_{in} \\ s &= a \oplus b \oplus c_{in} \\ &= a \cdot b \cdot c_{in} + \overline{c_{out}} \cdot (a + b + c_{in}) \end{aligned}$$


a	b	c <sub>in</sub>	c <sub>out</sub>	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



# 多位加法器结构



## Carry-Ripple Adder

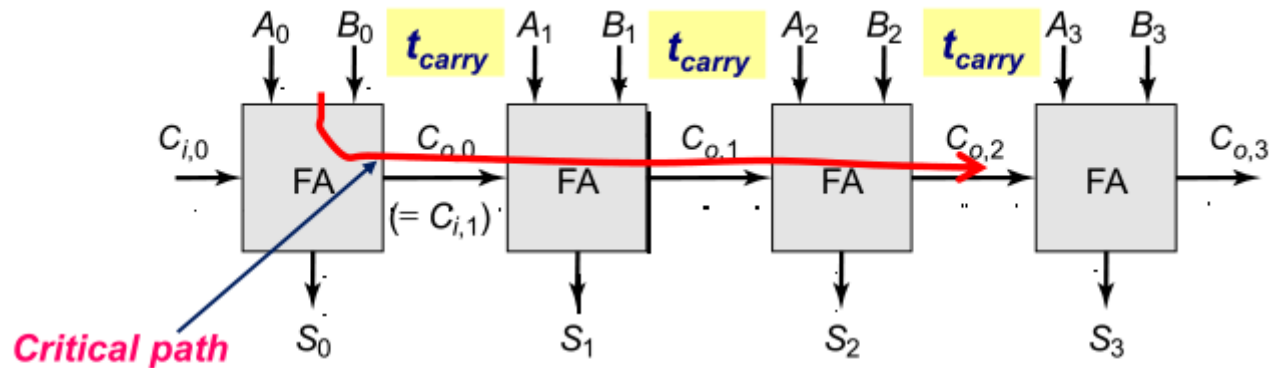


4-bit carry-ripple adder

*Worst-case propagation delay:*

$$t_{adder} = \underbrace{(N-1)t_{carry}} + t_{sum}$$



## GP Carry-Ripple Adder

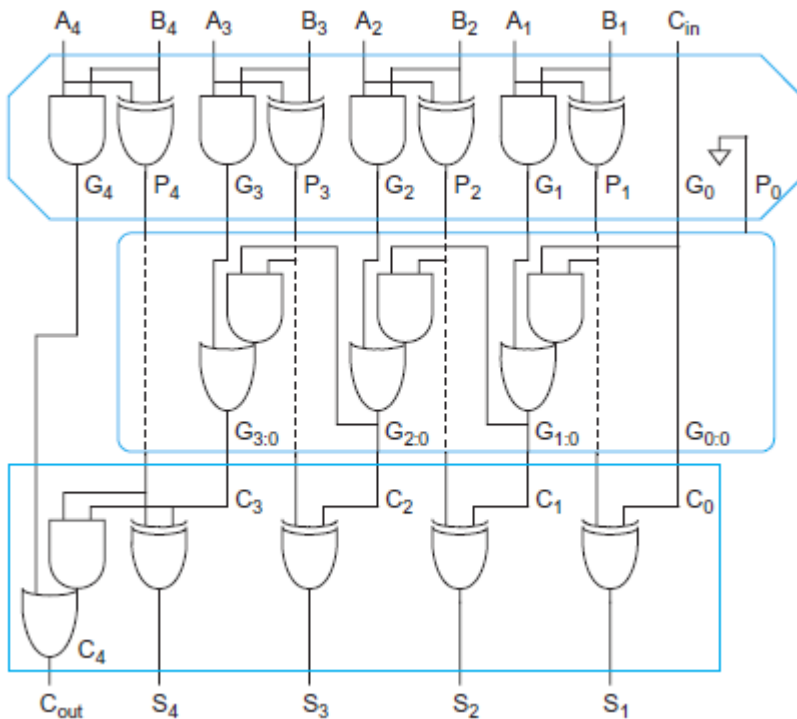

- $G_{n:0} = C_{o,n} = G_n + P_n \cdot C_{o,n-1}$
- $(G, P) \cdot (G', P') = (G + PG', PP')$
- $G_{i:j} = G_{i:k} + P_{i:k} \cdot G_{k-1:j}$
- $P_{i:j} = P_{i:k} \cdot P_{k-1:j}$
- $G_{i:i} = G_i = A_i \cdot B_i$
- $P_{i:i} = P_i = A_i \oplus B_i$
- $S_i = P_i \oplus G_{i-1:0}$
- $G_{0:0} = C_{in}$
- $P_{0:0} = 0$


4-bit carry-ripple adder using PG logic




# 多位加法器结构



## Carry-Select Adder



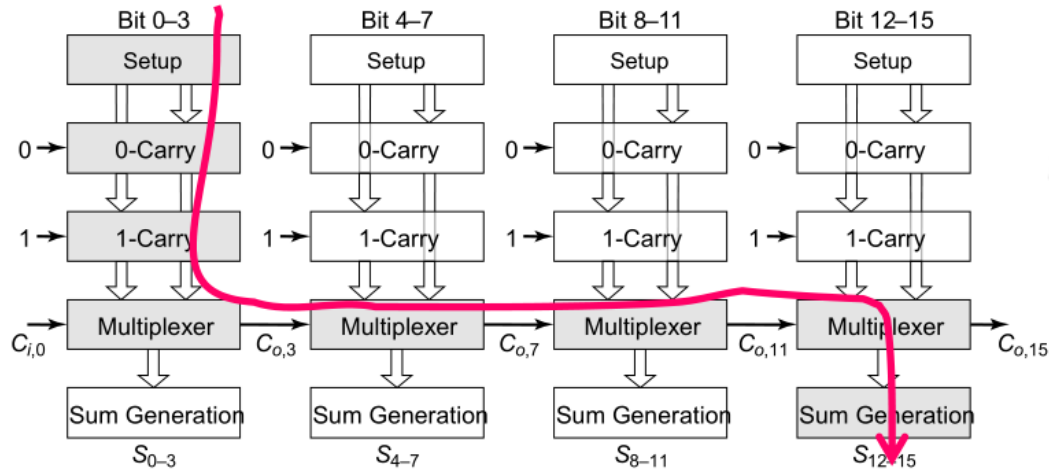

 
$$t_{add} = t_{setup} + M t_{carry} + \left( \frac{N}{M} \right) t_{mux} + t_{sum}$$






# 近似计算的应用需求

   






## Speculative Adder

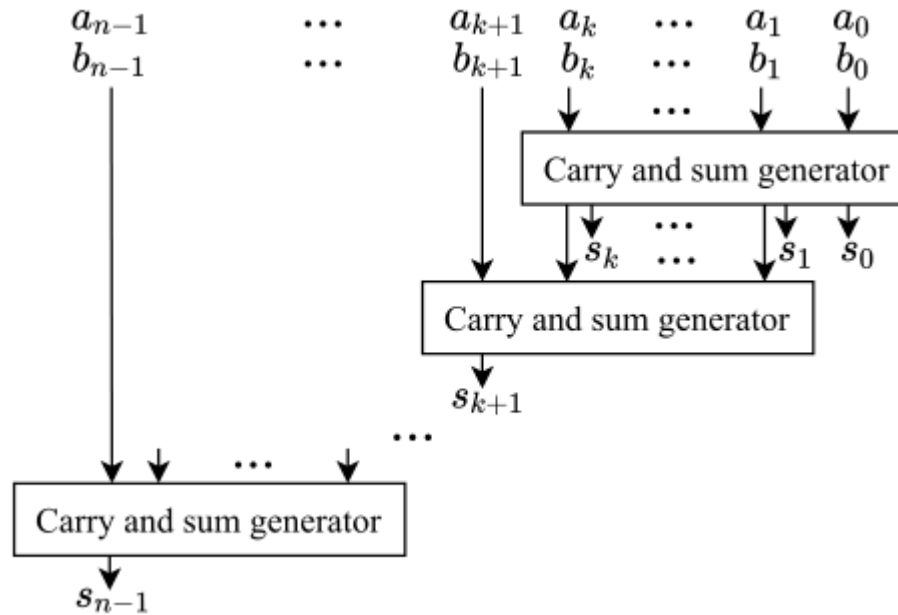

an n-bit speculative adder uses the previous k bits ( $k < n$ ) to predict the carry



## Segmented Adder

 



A segmented adder is implemented by several parallel subadder blocks with an independent carry-in



## 近似加法器结构



## Approximate Full Adder

 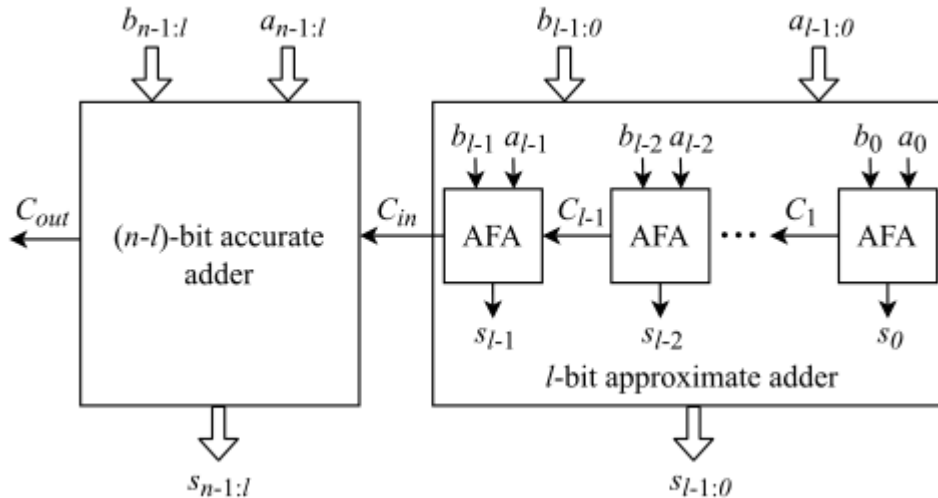

“Lower-Part-OR Adder(LOA)”


Approximate full adder is used to implement  $l$  LSBs in an  $n$ -bit adder ( $l < n$ ), whereas the  $(n-l)$  MSBs are computed by an Accurate adder




# 近似加法器结构



## Approximate Carry-Select Adder

 

Sum selection

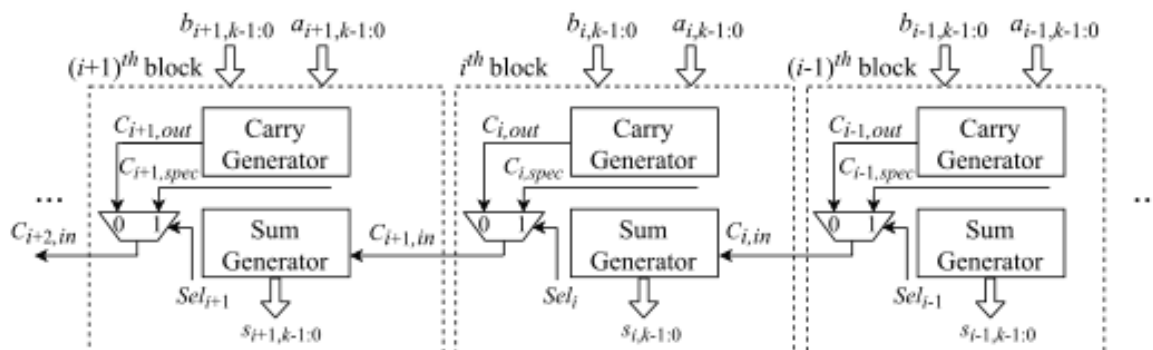

Carry-in selection



# 典型的近似加法器

-  RAP-CLA
-  ACAA
-  GeAr
-  HABA
-  SARA
-  RCPA
-  ETA-I/ETA-II
-  ...



# Outline



## 实验概述

- 加法器简介
- 近似计算加法器



## 实验要求

- 电路设计要求
- 报告要求



## 附录



# 项目要求

## 项目目标1: 设计一个 32-bit 无符号加法器 (作为baseline)

- 加法器结构可选择行波进位、超前进位等，也可根据文献选择其它结构；
- 搭建 SPICE 网表仿真测试，得到关键路径延迟和功耗等信息；（对功耗的测量**自行选取测试向量\***，提供了参考测试向量stimulus.vect见附件）

## 项目目标2: 设计一个 32-bit 无符号的**低功耗近似计算**加法器

- 自行查阅文献，选择合适（**错误率不高于 10%**）的近似加法器结构（在报告中指明设计结构及参考文献），搭建 SPICE 网表仿真测试；
- 优化选取结构的**关键路径延迟和功耗**；
- 与 baseline 进行功耗、延迟、漏电等各方面的比较，对近似加法器的优缺点进行讨论。（保持相同的测试向量）

\* **自选测试向量：** 需要说明选取的合理性



# 实验要求



## 需测量的参量

- **关键路径延时**：输入信号与输出信号50%翻转点间间隔（难点：**关键路径挑选，须在报告中述及**）
- **动态功耗**：基于自行选取测试向量测量平均动态功耗
- **泄漏功耗**：基于自行选取测试向量测量平均静态功耗
- **面积估计**： $\sum W \cdot L$ 或者粗略统计晶体管数量





# 实验要求



## 工艺

- 采用7nm PTM工艺库
- LP(low power)



## 仿真环境

- **输入信号上升下降时间:** 15ps
- **额定电压:** 0.7V
- **温度:** 25 °C
- **输出端口负载:** 8 倍最小尺寸 inverter 门电容负载
- **命名规则:** 输入与输出分别为A[31:0], B[31:0], SUM[32:0]



# 报告事宜



## 报告内容：

- 前期调研结果简述（结构选择，逻辑方式选择），明确设计目标  
和设计策略的选用
- SPICE网表描述，关键路径及data pattern选择
- 逻辑组织框图（标明关键路径）
- 优化设计方案（如sizing方案，设计技巧）
- 性能、功耗仿真结果分析
- 报告最后将电路网表贴出



## 提交方式：

- Canvas 平台
- **Deadline: 2022.x.xx**



# Outline



## 实验概览

- 加法器简介
- 近似计算加法器设计



## 实验要求

- 电路设计要求
- 报告要求



## 附录



## Digital vector file commands

- IO Syntax: IO I | O | B | U (信号方向输入、输出、双向、无用)
- VNAME: Syntax: VNAME  
vector\_name[[starting\_index:ending\_index]](定义向量名字)
- RADIX: Syntax: RADIX NUMBER\_OF\_BITS(定义每个向量bit数)
- PERIOD: Syntax: PERIOD TIME\_INTERVAL(定义数据表中数据间隔)
- TUNIT: Syntax:TUNIT [fs|ps|ns|us|ms] (定义VEC文件中时间单位)
- TEDLAY Syntax: TDELAY DELAY\_VALUE [MASK] (定义数据表中输入输出延时)
- VIL/VIH/VOH/VOL/VTH Syntax: keywords logic\_voltage [mask] (定义逻辑输入/输出低/高电平, 开关阈值)
- TFALL/TRISE/SLOPE: Syntax:keywords [trise|tfall] [mask] (定义输入信号斜率)



# 向量激励例子

## Digital Vector File Example

```

; specifies # of bits associated with each vector
radix 1 2 444
;*****
; defines name for each vector. For multi-bit vectors,
; innermost [] provide the bit index range, MSB:LSB
vname v1 va[[1:0]] vb[12:1]
;actual signal names: v1, va[0], va[1], vb1, vb2, ... vb12
;*****
; defines vector as input, output, or bi-directional
io i o bbb
; defines time unit
tunit ns
;*****
; vb12-vb5 are output when 'v1' is 'high'
enable v1 0 0 FF0
; vb4-vb1 are output when 'v1' is 'low'
enable ~v1 0 0 00F
;*****
; all signals have a delay of 1 ns
; Note: do not put the unit (such as ns) here again.
; HSPICE multiplies this value by the specified 'tunit'.
tdelay 1.0
; va[1] and va[0] signals have 1.5ns delays
tdelay 1.5 0 3 000
;*****
; specify input rise/fall times (if you want different
; rise/fall times, use the trise/tfall statement.)
; Note: do not put the unit (such as ns) here again.
; HSPICE multiplies this value by the specified 'tunit'.
slope 1.2
;*****
; specify the logic 'high' voltage for input signals
vih 3.3 1 0 000
vih 5.0 0 0 FFF
; to specify logic low, use 'vil'
;*****
; va & vb switch from 'lo' to 'hi' at 1.75 volts
vth 1.75 0 1 FFF

;*****
; tabular data section
10.0 1 3 FFF
20.0 0 2 AFF
30.0 1 0 888

```

## 施加测试向量:

- 1) 上述文件保存为stimulus.vect
- 2) 在testbench.sp中添加仿激励文件: .vec stimulus.vect
- 3) Testbench中对应的向量的激励即stimulus.vect中定义的数据表



# 参考文献

- ⑧ **TCASI 2018**, *Design and Evaluation of Approximate Logarithmic Multipliers for Low Power Error-Tolerant Applications*
- ⑧ **VLSI 2018**, *Systematic Design of an Approximate Adder The Optimized Lower Part Constant-OR Adder*
- ⑧ **TCASII 2018**, *RAP-CLA: A Reconfigurable Approximate Carry Look-Ahead Adder*
- ⑧ **VLSI 2020**, *An Efficient Parallel DA-Based Fixed Width Design for Approximate Inner-Product Computation*
- ⑧ **TCASII 2020**, *Stochastic Mixed-PR A Stochastically-Tunable Low-Error Adder*
- ⑧ **TCASI 2021**, *Accuracy-Configurable Radix-4 Adder With a Dynamic Output Modification Scheme*